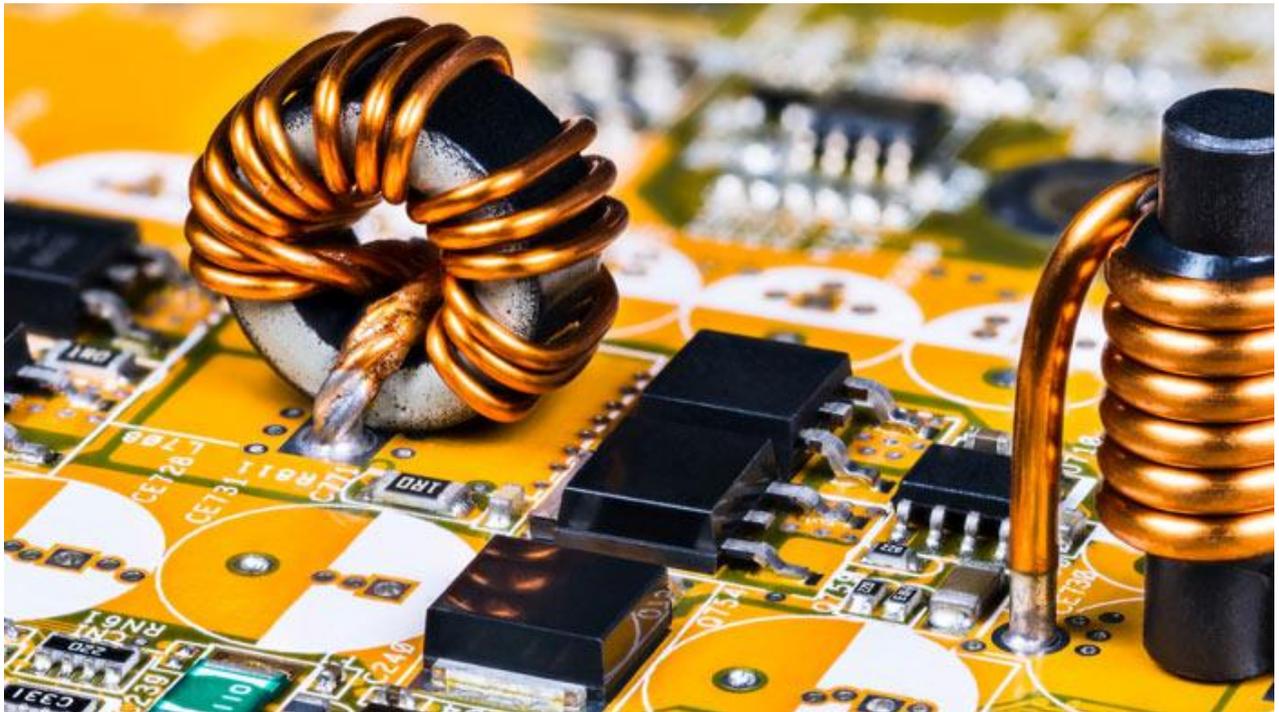


POWER ELECTRONICS

(EE3591, V SEMESTER – ELECTRICAL AND ELECTRONICS ENGINEERING,
As per Anna University 2021 Regulation)



Mr.O.RAJAGUNASEKARAN

Dr. S.RAJENDRAN

Dr .S. SAROJINI MARY

Mrs. JASMINE ARULARASI

Z Alpha Research and Publishing Hub™

Published and Printed by:

Z Alpha Research and Publishing Hub™

No. 14, Muthumanitwon, 3rd Cross, Senthaneerapuram,
Tiruchirappalli – 620 004.

Tamil Nadu, India.

Website: <https://zalpharph.in>

Email: zalpha.rph@gmail.com

Printed in India

Author Detail: Mr. O. Rajagunasekaran

Assistant Professor,

Department of Electrical and Electronics Engineering,

Mookambigai College of Engineering,

Pudukkottai District – 622 502,

Tamil Nadu, India.

Mobile: +91 9842527194

EE3591, POWER ELECTRONICS

**(V SEMESTER – ELECTRICAL AND ELECTRONICS
ENGINEERING,**

As per Anna University 2021 Regulation)

Mr.O.RAJAGUNASEKARAN

Assistant Professor, Department of EEE,
Mookambigai College of Engineering, Keeranur, Pudukkottai-Dt

Dr. S.RAJENDRAN

Professor, Department of EEE,
Mookambigai College of Engineering, Keeranur, Pudukkottai-Dt

Dr .S. SAROJINI MARY

Associate Professor, Department of EEE,
IndraGanesan College of Engineering, Manikandam, Trichy

Mrs. A. JASMINE ARULARASI

Assistant Professor, Department of EEE,
Oxford Engineering College, Pirattiyur, Trichy

Z Alpha Research and Publishing Hub TM

Tiruchirappalli – 620 004. Tamil Nadu. India.

Email: zalpha.rph@gmail.com

Email: orajagunasekaran@gmail.com

Cell: 9842527194

POWER ELECTRONICS

**Authors: Mr.O.Rajagunasekaran, Dr. S.Rajendran, Dr.S. SarojiniMary and
Mrs. A. Jasmine Arularasi**

Copyright © 2025, Z Alpha Research and Publishing Hub

All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means electronic, mechanical, photocopying, recording, or otherwise without the prior written permission of the publisher.

Published in 2025

ISBN:978-81-994040-7-6

Price: INR 320

Published and Printed by:

Z Alpha Research and Publishing Hub TM

No. 14, Muthumanitwon, 3rd Cross, Senthaneerpuram,
Tiruchirappalli – 620 004.

Tamil Nadu. India.

Website: <https://zalpharph.in>

Email: zalpha.rph@gmail.com

Printed in India

Author Detail: Mr. O. Rajagunasekaran

Assistant Professor,

Department of Electrical and Electronics Engineering,

Mookambigai College of Engineering,

Pudukkottai District – 622 502,

Tamil Nadu, India.

Mobile: +91 9842527194

Dedicated to

The God Almighty and

Our Family Members.

Preface

This book Power Electronics is a core subject for 5th semester Electrical and Electronics Engineering Department of Anna University affiliated colleges under 2021 regulation and it is an essential subject for all Universities syllabus. This covers various converters, Switching devices and its characteristics both static, dynamic, converter operation under various loads, Applications of various types of switches, rectifiers, voltage regulators and inverters.

This book consists of 5 units described below shortly.

Unit 1; This unit (Chapter 2) covers MOSFET dynamic behavior - driver and snubber circuits - low power high switching frequency switching Power supplies, buck, boost, buck-boost converters – Isolated topologies – resonant converters - switching loss calculations and thermal design.

Unit 2; This unit (Chapter 3) covers IGBT: Static and dynamic behavior - single phase half bridge and full bridge inverters - VSI :(1phase and three phase inverters square wave operation) - Voltage control of inverters single, multi pulse, sinusoidal, space vector modulation techniques – various harmonic elimination techniques-CSI.

Unit 3; This unit (Chapter 4) covers Power Diode – half wave rectifier – mid-point secondary transformer based full wave rectifier – bridge rectifier – voltage doubler circuit – distortion factor – capacitor filter for low power rectifiers – LC filters – Concern for power quality – three phase diode bridge.

Unit 4; This unit (Chapter 5) covers SCR-Two transistor analogy-based turn- ON – turn ON losses – thermal protection – controlled converters (1 pulse, 2 pulse, 3 pulse, 6 pulse) - displacement factor – ripple and harmonic factor - power factor mitigation, performance parameters – effect of source inductance - inverter angle limit.

Unit 5; This unit (Chapter 6) covers TRIAC triggering concept with positive and negative gate pulse triggering, TRIAC based phase controllers - various configurations for SCR based single and three phase controllers.

Mr.O.RAJAGUNASEKARAN

Dr.S.RAJENDRAN

Dr.S.SAROJINI MARY

Mrs. A. JASMINE ARULARASI

Acknowledgement

We express our heartfelt gratitude to **Tmt.R.Uma** Chairperson, **Thiru. D.Ravi**, Chief Executive, **Dr.P. Vasudevan**, Director, **Dr.R.Elangovan**, Principal, Head of the Department and colleagues of Mookambigai College of Engineering, Keeranur, Pudukkottai district.

We also thank our Chairman **Mr. T.Ganesan**, Secretary **Er.G.Rajasekaran**, Principal **Dr.G.Balakrishnan**, Head of the Department and colleagues of IndraGanesan College of Engineering, Manikandam, Trichy.

Our sincere gratitude to **Er.M.Subramaniam**, Chairman, **Dr.M.koilraj**, Principal, Head of the Department and colleagues of Oxford Engineering College, Pirattiyur, Trichy.

We would like to express our heartfelt thanks to Dr. G. Manickavasagam, Editor-in-Chief, Z Alpha Research and Publishing Hub, Trichy-4 for his sincere contribution in completion of this book.

Last but not least, we like to thank our family members and beloved friends for rendering their support to complete this book in successful manner.

Authors

Mr.O.RAJAGUNASEKARAN

Dr.S.RAJENDRAN

Dr.S. I. SAROJINI MARY

Mrs. A. JASMINE ARULARASI

CHAPTER – I

INTRODUCTION TO POWER ELECTRONICS

- 1.1. HISTORY OF POWER ELECTRONICS**
- 1.2. SOME APPLICATIONS OF POWER ELECTRONICS**
- 1.3. POWER ELECTRONIC APPLICATIONS**
 - 1.3.1. POWER SEMICONDUCTOR DEVICES**
- 1.4. POWER SEMICONDUCTOR DEVICES USED IN POWER ELECTRONICS**
- 1.5. VARIOUS TYPES OF POWER ELECTRONICS CONVERTERS**
 - 1.5.1. AC to DC Converters or Rectifiers**
 - 1.5.2. Uncontrolled Diode Rectifiers**
 - 1.5.3. Phase Controlled Rectifiers**
 - 1.5.4. DC to DC Converters**
 - 1.5.5. AC to AC Converters**
 - 1.5.6. AC/AC Voltage Converters**
 - 1.5.7. AC/AC frequency Converters**
 - 1.5.8. DC to AC Converters or Inverters**

CHAPTER – II

SWITCHING POWER SUPPLIES

- 1.6. MOSFET DYNAMIC BEHAVIOUR**
 - 1.6.1. Power MOSFET**
 - 1.6.2. Switching Characteristics of MOSFET**
 - 1.6.3. Advantages**
 - 1.6.4. Disadvantages**
 - 1.6.5 Applications**
- 2.2. MOSFET DRIVER AND SNUBBER CIRCUITS**
 - 2.2.1. Features of MOSFET drivers**
 - 2.2.2. Need for Gate drive circuit**
 - 2.2.3. Benefits of MOSFET drivers**
- 2.3. MOSFET SNUBBER CIRCUIT**
 - 2.3.1. Types of snubber circuits**
 - 2.3.2. Snubber circuit benefits**
- 2.4. LOW POWER HIGH SWITCHING FREQUENCY SWITCHING POWER SUPPLIES**
 - 2.4.1. Low Power High Frequency Power Supply**
 - 2.4.2. Fly-back Converter**
 - 2.4.3. Resonant Converter**
- 2.5. BUCK CONVERTER**
 - 2.5.1. Mode I: Switch is ON, Diode is OFF**
 - 2.5.2. Mode II: Switch is OFF, Diode is ON**
 - 2.5.3. Derivation for the output voltage**
 - 2.5.4. Advantages, Disadvantages and Applications**
- 2.6. BOOST CONVERTER**
 - 2.6.1. Mode I: Switch is ON, Diode is OFF**

- 2.6.2. Mode II : Switch is OFF, Diode is ON
- 2.6.3. Derivation for the output voltage
- 2.6.4. Advantages, Disadvantages and Applications
- 2.7. BUCK – BOOST CONVERTER
 - 2.7.1. Mode I: Switch is ON, Diode is OFF
 - 2.7.2. Mode II: Switch is OFF, Diode is ON
 - 2.7.3. Output waveforms
 - 2.7.4. Derivation for the output voltage
 - 2.7.5. Advantages, Disadvantages and Application
- 2.8. RESONANT CONVERTERS
 - 2.8.1. Principles of Resonant Converters
 - 2.8.2. Classification of Resonant Converters
 - 2.8.3. Zero Current Switching Resonant Converter (ZCS)
 - 2.8.3.1. L type ZCS Resonant Converter
 - 2.8.3.2. M type ZCS Resonant Converter
 - 2.8.4. Zero Voltage Switching Resonant Converter (ZVS)
 - 2.8.5. Applications of Resonant Converters
- 2.9. SWITCHING LOSS CALCULATIONS AND THERMAL DESIGN
 - 2.9.1. Conduction Losses
 - 2.9.2. Switching Loss
 - 2.9.3. Gate Circuit Loss

CHAPTER – III INVERTERS

- 3.1. IGBT: STATIC AND DYNAMIC BEHAVIOR
 - 3.1.1. Introduction
- 3.2. SINGLE PHASE HALF BRIDGE AND FULL BRIDGE INVERTERS
 - 3.2.1. Single Phase Half Bridge Inverter
 - 3.2.2. Single Phase Full Bridge Inverters
- 3.3. THREE PHASE INVERTERS
 - 3.3.1. 180 degree mode of Operation of 3 phase Inverter
 - 3.3.2. 120° mode of conduction of 3 phase Inverter
- 3.4. VOLTAGE CONTROL OF INVERTERS
(PULSE WIDTH MODULATION (PWM) TECHNIQUES)
 - 3.4.1. Introduction
- 3.5. TYPES OF PWM TECHNIQUES
 - 3.5.1. Single-Pulse Width Modulation
 - 3.5.2. Multiple-Pulse Width Modulation
 - 3.5.3. Sinusoidal Pulse Width Modulation (SPWM)
 - 3.5.4. Space-Vector Modulation
- 3.6. VARIOUS HARMONICS ELIMINATION TECHNIQUES
 - 3.6.1. Selective Harmonic Elimination (SHE)
 - 3.6.2. Multilevel Inverter For Selective Harmonic Elimination
 - 3.6.3. Harmonic Reduction By Transformer Method
 - 3.6.4. Other Transformer Methods
- 3.7. SINGLE-PHASE CURRENT SOURCE INVERTER

CHAPTER – IV UNCONTROLLED RECTIFIERS

- 4.1. POWER DIODES**
 - 4.1.1. DYNAMIC CHARACTERISTICS OF POWER SWITCHING DIODES**
 - 4.1.2. Power Diodes Types**
- 4.2. UNCONTROLLED RECTIFIERS**
 - 4.2.1. Half Wave Rectifier**
 - 4.2.2. Centre-Tapped Full Wave Rectifier**
 - 4.2.3. Bridge Rectifier Full Wave Rectifier**
- 4.3. VOLTAGE DOUBLER**
 - 4.3.1. Half Wave Voltage Doubler**
 - 4.3.2. Full Wave Voltage Doubler**
- 4.4. DISTORTION FACTOR**
- 4.5. CAPACITOR FILTER FOR LOW POWER RECTIFIERS**
 - 4.5.1. Full Wave Rectifier with Capacitor Filter**
 - 4.5.2. LC FILTER**
- 4.6. CONCERN FOR POWER QUALITY**
- 4.7. THREE PHASE DIODE BRIDGE RECTIFIER**
 - 4.7.1. Three Phase Half Wave Rectifier**
 - 4.7.2. Three Phase Full Wave Rectifier**

CHAPTER – V CONTROLLED RECTIFIERS

- 5.1. SILICON CONTROLLED RECTIFIER (SCR)**
 - 5.1.1. Static (V-I) Characteristics of SCR**
 - 5.1.2. Dynamic or switching characteristics of SCR**
 - 5.1.3. Turn ON methods of an SCR**
- 5.2. TWO TRANSISTOR ANALOGY OF SCR**
- 5.3. TURN ON LOSSES OF SCR**
- 5.4. THERMAL PROTECTION OF SCR**
- 5.5. CONTROLLED CONVERTERS (1 PULSE, 2 PULSE, 3 PULSE, 6 PULSE)**
 - 5.5.1. Single Phase Half Wave controlled Rectifier (1 Pulse Converter)**
 - 5.5.2. Single-phase Half Wave Controlled Rectifier with RL Load**
 - 5.5.3. Single Phase Full Wave Controlled Rectifier (or Converter)- 2 Pulse Converter**
 - 5.5.4. With Inductive Load**
 - 5.5.5. Single-Phase Bridge Converter (B-2 Connection)- 2 Pulse Converter**
 - 5.5.6. Single Phase Half Controlled Bridge Rectifier or Semi converter: 2 Pulse Converter**
 - 5.5.7. Three Phase Half Controlled Rectifier – 3 pulse converters**
 - 5.5.8. Three Phase Half Controlled Converter – 3 Pulse Converter**
 - 5.5.9. 3 Phase Fully Controlled Converter - 6 Pulse Converter**
- 5.6. DISPLACEMENT FACTOR**
- 5.7. RIPPLE AND HARMONIC FACTOR**
- 5.8. HARMONIC FACTOR**
- 5.9. POWER FACTOR MITIGATION**
- 5.10. PERFORMANCE PARAMETERS**

5.11. EFFECT OF SOURCE INDUCTANCE

5.11.1. Effect of Source Inductance in Single phase full converter

5.11.2. Effect of Source Inductance in 3 phase full converter

5.12. INVERTER ANGLE LIMIT

CHAPTER VI AC PHASE CONTROLLERS

6.1. INTRODUCTION

6.1.1. Construction of TRIAC

6.1.2. Modes of operation

6.1.3. V-I Characteristics of TRIAC

6.1.4. Applications of TRIAC

6.2. TRIAC BASED PHASE CONTROLLERS

6.2.1. Basic TRIAC Switching Circuit

6.2.2. Modified Switching Circuit

6.2.3. TRIAC Phase Control

6.2.4. Issues with TRIAC Circuits & the Solutions

6.3. VARIOUS CONFIGURATIONS FOR SCR BASED SINGLE AND THREE-PHASE CONTROLLERS

6.3.1. Single Phase Half Wave AC Voltage Controller

6.3.2. Single Phase Full Wave AC Voltage Controller

6.3.2.1. Single Phase Full Wave AC Voltage Controller with Resistive Load

6.3.2.2. Single Phase Full Wave AC Voltage Controller with RL Load

6.3.3. Three-phase, Three-wire AC Regulator with Balanced Resistive Load

6.3.4. Types of Loads and their Effects